

## **-: Additional Project Guidelines :-**

**Note : You need to connect output transformer that should be the half of the DC voltage applied to MOSFET's H\_Bridge voltage in order to get AC Voltage of your need (220 or 230).**

**And also please refer to the datasheet of the EGS002 module for more details on this project.**

**Some examples as :**

**A) 12 Volt battery - 6V Tranformer**

**B) 24 Volt battery - 12V Tranformer**

**C) 48 Volt battery - 24V Tranformer**